

# Contents

DEFINITIONS .....	1
<b>1 INTRODUCTION .....</b>	<b>9</b>
1.1 Aim of this book.....	9
1.2 Application area of electron tubes.....	10
1.3 Audio amplifiers versus instrumental amplifiers .....	10
1.4 Short history .....	11
1.5 Coding of electron tubes .....	13
1.6 Bibliography for chapter 1 .....	13
<b>2 PRINCIPLES OF ELECTRON EMISSION .....</b>	<b>14</b>
2.1 Types of electron emission.....	14
2.2 Space charge.....	15
2.3 Emission efficiency .....	16
2.4 Bibliography for chapter 2 .....	17
<b>3 DIODE.....</b>	<b>18</b>
3.1 The construction of diodes with directly and indirectly heated cathodes .....	18
3.2 Operation of diodes .....	19
3.3 Types of diodes and their application .....	20
3.4 Measuring of diode characteristics.....	21
3.5 Application of the diode as rectifier.....	31
3.5.1 Half-wave rectifier with buffer capacitor .....	31
3.5.2 Full-wave rectifier with buffer capacitor .....	33
3.5.3 Matching the diode rectifier with the supply transformer.....	35
3.5.4 Smoothing filters .....	40
3.5.4.1 $\pi$ -filter C-R-C .....	40
3.5.4.2 $\pi$ -filter C-L-C .....	42
3.5.5 Full-wave rectifier without buffer capacitor .....	46
3.5.6 Measurement of tube rectifier circuits .....	51
3.5.6.1 The practical test circuit .....	51
3.5.6.2 Analysis of the ripple voltage and output voltage as a function of the current in relation to the buffer capacitor and full/half-wave rectification.....	55
3.5.6.3 Analyses of the ripple voltage as function of the values of the $\pi$ -filter C-R-C.....	65
3.5.6.4 Analyses of the ripple voltage as a function of the values of the $\pi$ -filter C-L-C .....	68
3.5.6.5 Analyses of the ripple voltage and output voltage as a function of the values of the full-wave tube rectifier circuit without buffer capacitor .....	70
3.5.6.6 Measurement of some rectifier circuits.....	73
3.6 Heater and negative bias supplies .....	80
3.7 Practical advice .....	85
3.8 Bibliography for chapter 3 .....	88
<b>4 TRIODES .....</b>	<b>89</b>
4.1 The construction of triodes with directly and indirectly heated cathodes.....	89
4.2 Operation of triodes.....	90
4.3 Static triode characteristics and triode quantities.....	98
4.3.1 Static triode characteristics.....	98
4.3.2 Anode static steepness.....	99
4.3.3 Anode amplification factor.....	100

4.3.4	Anode AC internal resistance.....	102
4.3.5	Control grid base.....	104
4.3.6	Barkhausen formula.....	104
4.3.7	Triode quantities versus anode current.....	105
4.3.8	Dissipation and power.....	108
4.3.9	Measured static triode characteristics for the electron tubes ECC81, ECC82 and ECC83.....	108
4.3.10	Calculated examples of static triode quantities.....	114
4.4	Dynamic triode characteristics with anode resistor.....	120
4.4.1	The theory of the dynamic triode characteristics with anode resistor.....	120
4.4.2	The practice of the dynamic triode characteristics with anode resistor.....	132
4.5	Observations on heater supplies for triodes.....	136
4.5.1	Heater supply observed for directly heated triodes.....	137
4.5.2	Heater supply observed for indirectly heated triodes.....	139
4.6	Low frequency amplification with resistor coupling.....	142
4.6.1	Automatic negative bias voltage.....	142
4.6.2	Control grid current.....	145
4.7	The theory and practice of the basic triode circuits.....	148
4.7.1	The theory of the basic cathode circuit.....	148
4.7.2	The theory of the basic anode circuit or cathode follower.....	150
4.7.3	The theory of the basic negative feedback circuit.....	152
4.7.4	The theory of the basic control grid circuit.....	159
4.7.5	The theory of the basic cascode circuit.....	162
4.7.6	The theory of the basic Series Regulated Push Pull circuit.....	165
4.7.7	Summary of basic triode circuits.....	168
4.7.8	The practice of basic triode circuits.....	170
4.8	Phase shifter circuits in both theory and practice.....	186
4.8.1	The transformer phase shifter.....	186
4.8.2	The cathodyne phase shifter.....	188
4.8.3	The cascade phase shifter.....	195
4.8.4	The differential amplifier phase shifter.....	196
4.8.5	The inverting stage phase shifter.....	202
4.8.6	The self-adjusting phase shifter.....	204
4.8.7	Summary of the phase shifters.....	206
4.9	The driver stages in both theory and practice.....	207
4.9.1	The cathode follower driver stage.....	207
4.9.2	The differential amplifier driver stage.....	209
4.9.3	The Series Regulated Push Pull driver stage.....	212
4.10	The triode power amplifiers.....	216
4.10.1	Classifications of triode power amplifiers.....	216
4.10.1.1	Classification of triode power amplifiers by classes.....	216
4.10.1.2	Classification of triode power amplifiers by negative bias voltage.....	217
4.10.1.3	Classification of triode power amplifiers by control grid current.....	218
4.10.1.4	Classification of triode power amplifiers by single ended and push pull.....	219
4.10.2	Output transformers for the audio frequency range.....	221
4.10.3	Loudspeaker impedance and damping factor.....	225
4.10.4	Resistive and inductive load lines.....	230
4.10.5	The theory of single ended triode power amplifiers.....	234
4.10.5.1	Probable maximum delivered power and probable efficiency.....	235
4.10.5.2	Powers and efficiency as functions of the control grid cathode AC voltage.....	241
4.10.5.3	Parallel operation of power triodes.....	244
4.10.5.4	Real maximum delivered power and real efficiency.....	246
4.10.6	The practice of single ended triode power amplifiers.....	259

4.10.6.1	Real maximum power and efficiency as functions of $r_a/r_i$ for fixed control grid cathode AC voltage .....	262
4.10.6.2	Real maximum power and efficiency as functions of $r_a/r_i$ for variable control grid cathode AC voltage .....	264
4.10.6.3	Measured power and measured efficiency as functions of the control grid cathode AC voltage .....	266
4.10.6.4	Power balance and efficiency at maximum delivered power .....	268
4.10.6.5	Measured resistive and inductive load lines .....	270
4.10.6.6	Design examples of single ended triode power amplifiers .....	272
4.10.7	The theory of push pull triode power amplifiers .....	280
4.10.7.1	The B.J. Thompson method .....	281
4.10.7.2	Push pull class A triode power amplifiers .....	285
4.10.7.3	Push pull class B triode power amplifiers .....	286
4.10.7.4	Push pull class AB triode power amplifiers .....	296
4.10.7.5	Advanced topics of triode power amplifiers which are difficult .....	298
4.10.8	The practice of push pull triode power amplifiers .....	303
4.10.8.1	Application of the B.J. Thompson method for classes A, B and AB .....	306
4.10.8.2	Measured powers and efficiency as functions of the control grid cathode AC voltage for classes A, B and AB .....	319
4.10.8.3	Power balance and efficiency at maximum delivered power for classes A, AB and B .....	325
4.10.8.4	Design examples of push pull triode power amplifiers .....	329
4.10.9	Summary of triode power amplifiers .....	339
4.10.10	Other power triodes .....	341
4.11	Bibliography for chapter 4 .....	344
<b>5</b>	<b>TETRODE .....</b>	<b>345</b>
5.1	The construction of tetrodes .....	345
5.2	Why the tetrode was developed .....	346
5.3	Operation of tetrodes .....	346
5.4	Beam Power tetrode .....	350
5.5	Circuits and calculations applied to tetrodes .....	353
5.6	Bibliography for chapter 5 .....	354
<b>6</b>	<b>PENTODE .....</b>	<b>355</b>
6.1	Introduction .....	355
6.2	The construction of pentodes .....	356
6.3	Operation of pentodes .....	358
6.4	Static pentode characteristics and pentode quantities .....	364
6.4.1	Static pentode characteristics .....	364
6.4.2	Anode static steepness .....	365
6.4.3	Anode amplification factor .....	368
6.4.4	Anode AC internal resistance .....	369
6.4.5	Screen grid static steepness .....	371
6.4.6	Screen grid amplification factor .....	372
6.4.7	Screen grid AC internal resistance .....	374
6.4.8	Barkhausen formulae .....	376
6.4.9	Control grid bases .....	377
6.4.10	Pentode quantities versus anode current .....	379
6.4.11	Dissipation and power at the anode and screen grid .....	385
6.4.12	Measured static pentode characteristics of the EF86 electron tube .....	387
6.4.13	Calculation examples of static pentode quantities .....	395
6.5	Dynamic pentode characteristics with anode external resistor .....	402

6.5.1	The theory of the dynamic pentode quantities with anode external resistor .....	402
6.5.2	Additional draft of the theory of the dynamic pentode .....	414
6.5.3	The practice of the dynamic pentode quantities with anode external resistor .....	420
6.6	First interim comparison between triodes and pentodes .....	428
6.7	Low frequency amplification with resistor coupling .....	430
6.7.1	Realization of the screen grid cathode DC voltage .....	430
6.7.2	The basic cathode circuit with automatic negative bias DC voltage in theory and practice....	433
6.8	The MU-stage.....	442
6.8.1	The theory of the MU-stage .....	442
6.8.2	A practical example of the MU-stage .....	444
6.9	Pentode power amplifiers.....	452
6.9.1	The theory of single ended pentode power amplifiers .....	452
6.9.1.1	Probable maximum delivered anode power and probable anode efficiency.....	453
6.9.1.2	Powers and efficiency as functions of the control grid cathode AC voltage .....	460
6.9.1.3	Real maximum delivered power and real efficiency.....	462
6.9.2	The practice of single ended pentode power amplifiers.....	466
6.9.2.1	Real maximum power and anode efficiency as function of $r_a/R_i$ .....	468
6.9.2.2	Measured power and efficiency as functions of the control grid cathode AC voltage .....	470
6.9.2.3	Power balance and efficiency at maximum delivered power.....	472
6.9.2.4	Design examples of single ended pentode power amplifiers .....	475
6.9.3	Second interim comparison between triodes and pentodes.....	480
6.9.4	The theory of push pull pentode power amplifiers .....	481
6.9.4.1	Push pull class A pentode power amplifiers .....	484
6.9.4.2	Push pull class B pentode power amplifiers.....	484
6.9.4.3	Push pull class AB pentode power amplifiers.....	495
6.9.4.4	Advanced topics of pentode power amplifiers which are difficult .....	496
6.9.5	The practice of push pull pentode power amplifiers .....	500
6.9.5.1	Design examples of a push pull pentode power amplifier .....	503
6.9.5.2	Real powers and efficiency as functions of control grid cathode AC voltage for classes A, B and AB .....	511
6.9.5.3	Power balance and efficiency with maximum delivered power for classes A, B and AB.....	518
6.9.6	Third interim comparison between triodes and pentodes.....	523
6.10	The ultra-linear power amplifier .....	525
6.10.1	The theory of ultra-linear power amplifiers .....	525
6.10.1.1	An adventure between triode and pentode .....	525
6.10.1.2	Powers and efficiency of ultra-linear power amplifiers .....	531
6.10.1.3	A network analysis of the ultra-linear power amplifier .....	534
6.10.2	The practice of ultra-linear power amplifiers.....	545
6.10.2.1	Determination of the screen grid primary transformer tap $x$ .....	545
6.10.2.2	The anode amplification and the AC output impedance as a function of the screen grid primary transformer tap $x$ .....	551
6.10.2.3	Practical comparison of a triode, an ultra-linear and a pentode power amplifier .....	557
6.10.2.4	The contributions of anode AC current and screen grid AC current to ultra-linear power.....	560
6.11	Summary of the pentode and the ultra-linear power amplifier .....	562
6.12	Bibliography for chapter 6 .....	563
<b>7</b>	<b>FREQUENCY DEPENDENT BEHAVIOUR .....</b>	<b>564</b>
7.1	Definition and concepts.....	564
7.2	Frequency dependent behaviour of the amplifier components .....	575
7.2.1	Frequency dependent behaviour of the output transformer .....	575
7.2.2	Frequency dependent behaviour of the passive components .....	580
7.2.3	Frequency dependent behaviour of the triode .....	586

7.2.4	Frequency dependent behaviour of the pentode.....	595
7.3	Amplification at low frequency signals .....	598
7.4	Amplification at high frequency signals .....	609
7.5	Amplification of low and high frequency signals .....	620
7.6	The practice of frequency dependent behaviour .....	632
7.6.1	Measurement of frequency characteristics .....	632
7.6.2	Checking a practical situation .....	637
7.7	Afterthought .....	649
7.8	Bibliography for chapter 7 .....	652
<b>8</b>	<b>NON-LINEAR DISTORTION AND NOISE .....</b>	<b>653</b>
8.1	The sound from electron tube amplifiers .....	653
8.2	Non-linear distortion already discussed .....	654
8.3	Harmonic analysis .....	656
8.4	Applied harmonic analysis .....	658
8.4.1	Harmonic analysis of the output transformer .....	658
8.4.2	Harmonic analysis of electron tubes .....	659
8.4.2.1	The curvature of the anode steepness characteristics .....	659
8.4.2.2	The algebraic determination of the coefficients of the power series.....	666
8.4.2.3	The graphical determination of the second and third harmonics .....	672
8.4.2.4	InterModulation Distortion IMD .....	681
8.4.3	Harmonic analysis of passive components.....	683
8.5	Prevention of non-linear distortion without feedback.....	685
8.5.1	The anode resistor against non-linear distortion .....	685
8.5.2	The push pull power amplifier against non-linear distortion .....	686
8.6	The practice of non-linear distortion.....	688
8.6.1	The spectrum analyzer, the pure signal source and the measurement in cascade.....	688
8.6.2	Non-linear distortion of passive components.....	692
8.6.3	Determination of the coefficients of the power series of the second and third harmonic.....	694
8.6.4	The impact of the anode resistor on non-linear distortion .....	700
8.6.5	The basic cathode circuit versus the basic SRPP circuit versus the MU-stage circuit.....	702
8.6.6	The basic cascode circuit versus the basic pentode circuit .....	705
8.6.7	Measured non-linear distortion of some known electron tube amplifiers.....	707
8.7	Afterthoughts on non-linear distortion.....	712
8.8	Noise.....	713
8.8.1	Thermal noise.....	713
8.8.2	Noise in electron tubes .....	715
8.8.3	Signal to noise ratio and noise factor .....	717
8.8.4	A little more about the practice of noise .....	718
8.9	Bibliography for chapter 8 .....	721
<b>9</b>	<b>NEGATIVE FEEDBACK.....</b>	<b>722</b>
9.1	Types of negative feedback.....	722
9.1.1	Negative parallel-serial feedback.....	722
9.1.2	Negative serial-serial feedback .....	723
9.1.3	Negative parallel-parallel feedback.....	724
9.1.4	Negative serial-parallel feedback.....	724
9.1.5	Negative voltage feedback .....	725
9.1.6	Negative current feedback.....	725
9.1.7	First summary of negative feedback .....	726
9.2	The impact of negative feedback .....	727
9.3	The impact of negative feedback on gain and input and output impedances.....	730

9.3.1	Calculations for negative parallel-series feedback.....	730
9.3.2	Calculations for negative serial-serial feedback.....	732
9.3.3	Calculations for negative parallel-parallel feedback.....	733
9.3.4	Calculations for negative serial-parallel feedback.....	735
9.3.5	Second summary of negative feedback.....	737
9.4	Calculations for application examples.....	738
9.5	The impact of negative feedback on disturbances and noise.....	752
9.6	The impact of negative feedback on the frequency characteristics.....	754
9.6.1	The impact of negative feedback at lower frequencies.....	754
9.6.2	The impact of negative feedback at higher frequencies.....	755
9.6.3	The impact of negative feedback at lower and higher frequencies.....	757
9.6.4	The impact of negative feedback on a cascade of amplifier stages.....	758
9.6.5	Frequency independent and frequency dependent negative feedback parts.....	762
9.6.6	Discussion of the emergence of a new theory for negative feedback.....	763
9.6.7	Stability and the Nyquist diagram.....	770
9.7	Negative feedback between power tubes and the output transformer.....	772
9.8	The impact of negative feedback on the quantities of the sound.....	774
9.9	The practice of negative feedback.....	774
9.9.1	The practical test circuits.....	774
9.9.2	Negative-feedback amplification as a function of the negative-feedback voltage ratio.....	778
9.9.3	The crossover points as a function of the negative-feedback voltage ratio.....	781
9.9.4	Harmonic distortion visually observed as a function of the negative-feedback voltage ratio ..	782
9.9.5	The harmonics as a function of the output power versus negative-feedback voltage ratio .....	783
9.9.6	Total Harmonic Distortion as a function of negative-feedback voltage ratio mathematically .	786
9.9.7	The reduction of the crossover distortion for class B push pull amplifiers.....	787
9.10	Bibliography for chapter 9.....	789
<b>10</b>	<b>THE CONSTRUCTION OF ELECTRON TUBE AMPLIFIERS .....</b>	<b>790</b>
10.1	Introduction.....	790
10.2	Electronic components.....	790
10.3	Connection and assembly materials.....	792
10.4	Electrical construction methods.....	796
10.4.1	Construction on tagboards.....	796
10.4.2	Construction ‘in the air’.....	799
10.4.3	Construction on breadboard print.....	801
10.4.4	Construction on printed circuit board.....	804
10.5	Experimental set-ups.....	805
10.6	Electro Magnetic Compatibility EMC.....	807
10.6.1	Crosstalk.....	807
10.6.2	Supply distribution.....	811
10.6.3	Grounding.....	812
10.6.4	Shielding.....	812
10.7	Safety.....	813
10.8	Cooling.....	814
10.9	Vendors for components and sources of knowledge.....	815
10.10	Design strategies.....	816
10.11	Bibliography for chapter 10.....	818
<b>INDEX.....</b>		<b>819</b>